NEET UG TARGET | PHYSICS • CLASS 12 | UNIT II: CURRENT ELECTRICITY

HIGH-YIELD COMPREHENSIVE GUIDE

Current Electricity: Master Tutorial & Complete Assessment

Complete theoretical foundation, microscopic electron dynamics, circuit analysis laws, and exam-standard practice problems for NEET UG aspirants.

1. Syllabus Blueprint & Learning Objectives

Current Electricity is one of the highest-weightage topics in the NEET UG Physics syllabus, consistently accounting for 3 to 4 questions (12 to 16 marks) in the examination. The subject bridges microscopic charge-carrier dynamics with macroscopic circuit principles, demanding both conceptual clarity and rapid, error-free numerical problem-solving skills.

NEET UG Strategic Blueprint & Trends

NEET UG questions in this unit primarily emphasize:

- **Microscopic parameters:** Calculations connecting drift velocity, current density, mobility, and relaxation time.
- **Dimensional and geometric variations:** The effect of wire stretching, drawing, and temperature variation on resistance and resistivity.
- **Non-Ohmic materials:** Identifying characteristic curves of junction diodes, thermistors, and materials displaying negative differential resistance like Gallium Arsenide (GaAs).
- **Cell combinations:** Grouping of identical and non-identical cells in series and parallel, including terminal potential difference under discharging vs. charging conditions.
- **Circuit simplification:** Systematic application of Kirchhoff's Junction and Loop Rules, and rapid reduction of symmetrical and Wheatstone bridge networks.

Key Learning Outcomes

Upon completing this tutorial, you will be able to:

1. Distinguish between steady and instantaneous currents and compute current density as a vector field.
2. Derive microscopic expressions for electrical conductivity (σ) and resistivity (ρ) using the free-electron gas model.
3. Quantify the temperature dependence of resistance across conductors, standard alloys, semiconductors, and insulators.
4. Analyze electrochemical cells, calculate internal resistance, and evaluate terminal voltage across active and passive branches.
5. Formulate independent loop and node equations using Kirchhoff's laws to solve multiloop networks.
6. Determine the balance condition of a Wheatstone bridge and exploit circuit symmetry for high-speed problem solving.

2. Electric Current and Current Density

2.1 Definition of Electric Current

In electrostatics, all electric charges are considered to be at rest. When charges are placed in motion, their collective transport constitutes an **electric current**. Natural manifestations include atmospheric lightning

discharges, where charge transfer is transient and non-steady. In contrast, steady currents are established in closed direct-current (DC) circuits powered by galvanic cells or batteries.

Consider an arbitrary cross-sectional area oriented normal to the direction of charge motion. In a given time interval t, let q_+ represent the net quantity of positive charge passing through the area in the forward direction (i.e., forward flow minus backward flow), and let q_- represent the net negative charge passing forward. The net forward charge transfer q across the area is:

$$q = q_+ - q_-$$

For a steady current, the charge transported is directly proportional to time. The steady electric current I is defined as:

$$I = \frac{q}{t}$$

If the flow of charge varies with time, we define the **instantaneous electric current** $I(t)$ as the differential limit of the charge ΔQ transferred during an infinitesimal time interval Δt:

$$I(t) = \lim_{\Delta t \to 0} \frac{\Delta Q}{\Delta t} = \frac{dQ}{dt}$$

Conversely, the total charge Q transported across a cross-section between time t_1 and t_2 is obtained by integrating the current:

$$Q = \int_{t_1}^{t_2} I(t)\, dt$$

BOSONANCE

2.2 Units and Scalar Nature of Current

In the International System of Units (SI), the unit of electric current is the **ampere (A)**, which is one of the fundamental SI base units. One ampere corresponds to the transport of one coulomb of charge per second ($1\,\mathrm{A} = 1\,\mathrm{C\,s^{-1}}$).

Current Regime	Typical Order of Magnitude	Physical Context
Atmospheric Lightning	$10^4\,\mathrm{A}$ to $10^5\,\mathrm{A}$	Massive non-steady cloud-to-ground dielectric breakdown
Household Appliances	$0.1\,\mathrm{A}$ to $15\,\mathrm{A}$	Electric toasters, room heaters, lighting circuits
Semiconductor Electronics	$10^{-3}\,\mathrm{A}$ (mA) to $10^{-6}\,\mathrm{A}$ (μA)	Integrated circuits, sensor interfaces, microcontrollers
Human Nervous System	$10^{-6}\,\mathrm{A}$ (μA) to $10^{-9}\,\mathrm{A}$ (nA)	Biological action potentials and synaptic transmissions

> **Scalar Nature of Electric Current**
>
> Although we assign direction arrows to electric currents in circuit schematics, **electric current is a scalar quantity**. It does not follow the parallelogram law or triangle law of vector addition. When two conductor wires carrying currents I_1 and I_2 meet at an arbitrary angle θ, the total outgoing current is simply the algebraic sum $I = I_1 + I_2$, totally independent of the spatial orientation angle θ.

2.3 Current Density Vector (j)

To characterize the microscopic distribution of current within a medium, we define the **current density vector** $\mathbf{j}$. At any given point inside a conductor, current density is defined as the current flowing per unit cross-sectional

area taken perpendicular to the direction of charge flow:

$$j = \frac{I}{A_{\perp}}$$

Current density is a genuine vector quantity. Its magnitude is $I/A_{\perp}$ and its direction points along the local electric field $\mathbf{E}$ (the direction along which positive test charges would drift). If an elementary surface vector $d\mathbf{S}$ is inclined at an angle θ to $\mathbf{j}$, the current dI crossing the area is the scalar dot product:

$$dI = \mathbf{j} \cdot d\mathbf{S} = j\, dS \cos\theta \implies I = \int_S \mathbf{j} \cdot d\mathbf{S}$$

The SI unit of current density is **ampere per square metre** ($\mathrm{A\,m^{-2}}$), with dimensional formula $[\mathrm{M^0 L^{-2} T^0 A^1}]$.

3. Mechanism of Electric Conduction: Drift Velocity, Relaxation Time, and Mobility

3.1 Microscopic Picture of a Metallic Conductor

In solid metallic crystals (such as copper, aluminum, or silver), valence electrons are detached from parent atoms to form an electron gas that moves freely within the fixed positive ion lattice. A cubic metre of a typical metal contains an enormous electron density, $n \approx 10^{28}$ to $10^{29}\ \mathrm{m^{-3}}$.

In the **absence of an applied electric field**, conduction electrons execute chaotic thermal motion, undergoing continuous elastic collisions with the vibrating lattice ions. By the equipartition theorem, the thermal speed v_{th} at temperature T is:


$$\frac{1}{2} m v_{\mathrm{th}}^2 = \frac{3}{2} k_{\mathrm{B}} T \implies v_{\mathrm{th}} \approx \sqrt{\frac{3 k_{\mathrm{B}} T}{m}} \approx 10^5\ \mathrm{m\,s^{-1}} \quad (\text{at } 300\,\mathrm{K})$$

Immediately after any collision, the rebound direction of an electron is completely isotropic and random. Averaging over the macroscopic population of N free electrons, the vector sum of thermal velocities vanishes identically:

$$\langle \mathbf{v} \rangle = \frac{1}{N} \sum_{i=1}^{N} \mathbf{v}_i = 0$$

Consequently, there is no preferential direction of charge transport, and the net electric current in an isolated conductor is strictly zero.

BOSONANCE

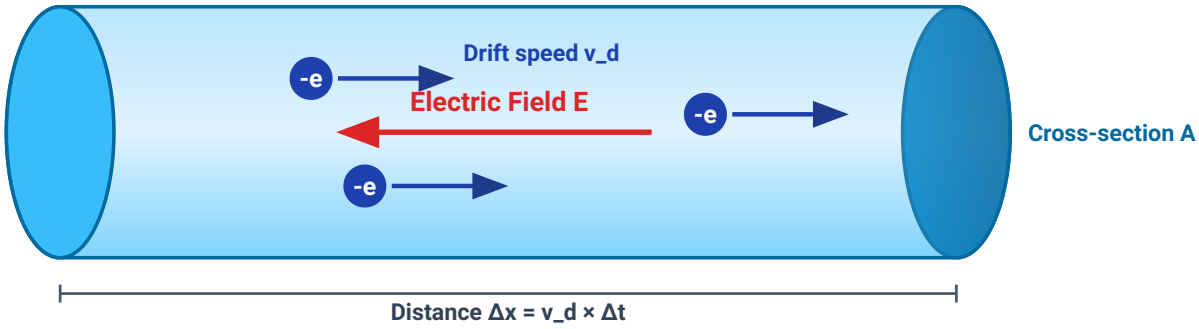

Tutorial Diagram 1: Transport of mobile electrons across cross-sectional area A under an applied electric field $\mathbf{E}$. The drift velocity $\mathbf{v}_d$ is oriented opposite to $\mathbf{E}$.

3.2 Derivation of Electron Drift Velocity and Relaxation Time

When a steady electric field $\mathbf{E}$ is maintained along the conductor, every conduction electron experiences a constant electrostatic force $\mathbf{F} = -e\mathbf{E}$. The resulting instantaneous acceleration $\mathbf{a}$ between collisions is:

$$\mathbf{a} = \frac{\mathbf{F}}{m} = -\frac{e\mathbf{E}}{m}$$

where $e = 1.6 \times 10^{-19}\,\mathrm{C}$ is the elementary charge magnitude and $m = 9.11 \times 10^{-31}\,\mathrm{kg}$ is the electron mass.

Consider the ith electron. If its velocity immediately following its most recent collision was $\mathbf{v}_i$, and t_i is the elapsed time since that collision, its velocity $\mathbf{V}_i$ at time t is governed by kinematics:

$$\mathbf{V}_i = \mathbf{v}_i + \mathbf{a}t_i = \mathbf{v}_i - \frac{e\mathbf{E}}{m}t_i$$


To obtain the net macroscopic velocity, we compute the ensemble average over all N electrons. Since the initial velocities $\mathbf{v}_i$ emerge randomly in all directions after collisions, $\langle \mathbf{v}_i \rangle = 0$. The average elapsed time $\langle t_i \rangle$ represents the **mean relaxation time** τ (the average time elapsed between two successive electron-ion collisions, typically $\tau \approx 10^{-14}\,\mathrm{s}$).

$$\mathbf{v}_d = \langle \mathbf{V}_i \rangle = \langle \mathbf{v}_i \rangle - \frac{e\mathbf{E}}{m}\langle t_i \rangle = -\frac{e\mathbf{E}}{m}\tau$$

The magnitude of the drift speed is thus:

$$v_d = \frac{eE\tau}{m}$$

BOSONANCE

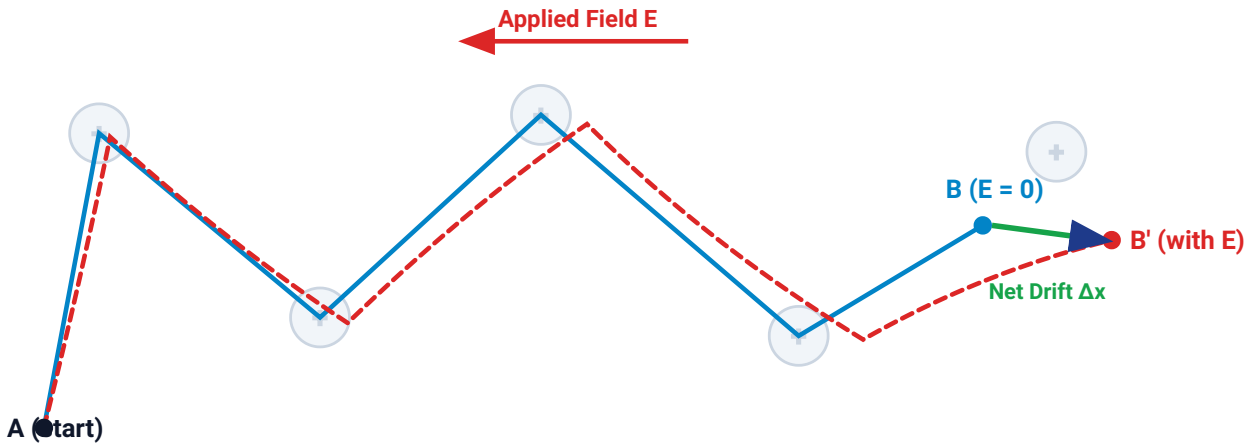

Tutorial Diagram 2: Microscopic electron trajectory. Solid blue lines trace straight paths during purely thermal motion ($\mathbf{E} = 0$). Dashed red paths show curved segments under an applied electric field $\mathbf{E}$, producing a small net displacement BB' opposite to $\mathbf{E}$.

3.3 Relation Between Drift Speed and Electric Current

Consider a segment of a uniform conductor of cross-sectional area A carrying an electron number density n. During a short time interval Δt, all free electrons located within a distance $\Delta x = v_d \Delta t$ to the left of cross-section A will cross it.

The total number of electrons in this cylindrical volume is:

$$\Delta N = n \times \text{Volume} = n A v_d \Delta t$$

Since each electron carries charge $q = -e$, the magnitude of charge ΔQ crossing area A in time Δt is:

$$\Delta Q = \Delta N \times e = n e A v_d \Delta t$$

Hence, the electric current $I = \Delta Q / \Delta t$ is:

$$I = n e A v_d$$

Dividing by cross-sectional area A, the current density j is:

$$j = \frac{I}{A} = n e v_d$$

Expressed in vector notation, noting that electrons carry negative charge ($q = -e$) and velocity $\mathbf{v}_d$:

$$\mathbf{j} = -n e \mathbf{v}_d$$

3.4 Electron Mobility (μ)

The ease with which charge carriers drift in a material under the influence of an electric field is quantified by their **mobility (μ)**. Mobility is defined as the magnitude of drift velocity acquired per unit applied electric field:

BOSONANCE

$$\mu = \frac{|\mathbf{v}_d|}{E}$$

Substituting $v_d = \frac{eE\tau}{m}$, we obtain:

$$\mu = \frac{e\tau}{m}$$

Units and Dimensions of Mobility

- **SI Unit:** $\mathrm{m^2\,V^{-1}\,s^{-1}}$ or $\mathrm{m\,s^{-1}/(N\,C^{-1})} = \mathrm{m^2\,A\,N^{-1}\,s^{-1}}$.
- **Practical Unit:** $\mathrm{cm^2\,V^{-1}\,s^{-1}}$, where $1\,\mathrm{m^2\,V^{-1}\,s^{-1}} = 10^4\,\mathrm{cm^2\,V^{-1}\,s^{-1}}$.
- **Dimensional Formula:** $[\mathrm{M^{-1}L^0T^2A^1}]$.
- **Sign Convention:** Mobility is defined as a **strictly positive scalar quantity** for all types of charge carriers (electrons, holes, or positive/negative ions).

3.5 The Three Characteristic Speeds in Electrical Conduction

A frequent conceptual hurdle for NEET aspirants is understanding why light bulbs turn on virtually instantly when switched on, despite electron drift velocities being remarkably slow. It is essential to distinguish between three distinct physical speeds:

Characteristic Speed	Symbol / Formula	Typical Magnitude	Physical Nature & Role
Drift Speed	$v_d = \frac{I}{neA}$	$\sim 10^{-4}$ to $10^{-3}\,\mathrm{m\,s^{-1}}$ ($\sim 1\,\mathrm{mm\,s^{-1}}$)	Extremely slow net directional migration of electrons superposed onto random thermal motion.
Random Thermal Speed	$v_{\mathrm{th}} \approx \sqrt{\frac{3k_{\mathrm{B}}T}{m}}$	$\sim 10^5\,\mathrm{m\,s^{-1}}$ (at $300\,\mathrm{K}$)	Chaotic kinetic speed of electrons between collisions. Averages out to zero vector displacement.
Electromagnetic Wave Signal Speed	$c \approx 3 \times 10^8\,\mathrm{m\,s^{-1}}$	Speed of light ($\sim 10^8\,\mathrm{m\,s^{-1}}$)	Rate at which the electric field establishes itself along the conductor, setting all local electrons into motion almost instantaneously.

4. Ohm's Law and Microscopic Derivation of Resistivity

4.1 Macroscopic Form of Ohm's Law

Formulated by Georg Simon Ohm in 1828, Ohm's law asserts that: *At constant physical conditions (especially temperature, mechanical strain, and pressure), the electric current I flowing through a conductor is directly proportional to the potential difference V maintained across its terminals.*

$$V \propto I \implies V = RI$$

where the constant of proportionality R is the **electrical resistance** of the conductor. In the SI system, resistance is measured in **ohms (Ω)**, where $1\,\Omega = 1\,\mathrm{V\,A^{-1}}$. The dimensional formula of resistance is $[\mathrm{M^1L^2T^{-3}A^{-2}}]$.

4.2 Geometric Dependence of Resistance

Resistance depends both on the intrinsic material property and the external physical dimensions of the conductor:

BOSONANCE

1. **Length (l):** Joining two identical conductors of length l and area A end-to-end creates a conductor of length $2l$. The total voltage required to maintain current I is $2V$, so $R_{\text{new}} = 2V/I = 2R$. Hence, resistance is proportional to length:
$$R \propto l$$
2. **Cross-sectional Area (A):** Dividing a slab of area A lengthwise into two identical halves of area $A/2$ means each half carries current $I/2$ under potential V. The resistance of each half is $R_{\text{half}} = V/(I/2) = 2R$. Hence, resistance is inversely proportional to area:
$$R \propto \frac{1}{A}$$

Combining these two relationships yields:

$$R = \rho \frac{l}{A}$$

where ρ is the **electrical resistivity** (or specific resistance) of the material. Resistivity is an intrinsic property that depends on the substance, temperature, and pressure, but is strictly independent of the conductor's geometrical dimensions (length and area).

The reciprocal of resistivity is called **electrical conductivity** (σ):

$$\sigma = \frac{1}{\rho}$$

The SI unit of resistivity is **ohm-metre** ($\Omega\,\mathrm{m}$) $[\mathrm{M^1L^3T^{-3}A^{-2}}]$, and the SI unit of conductivity is **siemens per metre** ($\mathrm{S\,m^{-1}}$ **or** $\Omega^{-1}\,\mathrm{m^{-1}}$).

4.3 Microscopic Derivation of Ohm's Law

We can establish the theoretical foundation of Ohm's law by linking the microscopic drift velocity to the macroscopic electric field. Recall that:

$$j = nev_d \quad \text{and} \quad v_d = \frac{eE\tau}{m}$$

Substituting the drift speed expression into the current density equation gives:

$$j = ne\left(\frac{eE\tau}{m}\right) = \left(\frac{ne^2\tau}{m}\right)E$$

Since the vectors $\mathbf{j}$ and $\mathbf{E}$ are collinear, we express this in full vector form as:

$$\mathbf{j} = \sigma\mathbf{E} \quad \text{or} \quad \mathbf{E} = \rho\mathbf{j}$$

This is the **microscopic (vector) statement of Ohm's law**. Comparing coefficients yields the fundamental microscopic expressions for conductivity and resistivity:

$$\sigma = \frac{ne^2\tau}{m} \quad \text{and} \quad \rho = \frac{m}{ne^2\tau}$$

BOSONANCE

High-Yield NEET Formula: Stretching / Drawing of Wires

When a wire of mass M, volume $V = A \cdot l$, and density d is stretched or drawn uniformly without loss of material, its **volume remains constant** ($A \cdot l = \text{constant}$).

- If length increases by a factor k ($l' = kl$), then area decreases by k ($A' = A/k$), so:

$$R' = \rho \frac{l'}{A'} = \rho \frac{kl}{A/k} = k^2 R$$

- In terms of radius r or diameter D, since $A = \pi r^2$, constant volume implies $l \propto 1/r^2$, leading to:

$$R \propto \frac{l}{A} \propto \frac{1/r^2}{r^2} \propto \frac{1}{r^4} \implies \frac{R'}{R} = \left(\frac{r}{r'}\right)^4$$

- **Small percentage changes:** For fractional elongation $\Delta l/l \leq 5\%$, differentiating $R = \rho l^2/V$ yields:

$$\frac{\Delta R}{R} \approx 2\frac{\Delta l}{l} \approx -4\frac{\Delta r}{r}$$

5. Temperature Dependence of Electrical Resistivity

5.1 General Mathematical Formulation

Over moderate temperature intervals, the electrical resistivity of metallic conductors increases approximately linearly with temperature:

$$\rho(T) = \rho_0[1 + \alpha(T - T_0)]$$

where ρ_0 is the resistivity at reference temperature T_0 (commonly $0\,^\circ\text{C}$ or $20\,^\circ\text{C}$ / $273.15\,\text{K}$), and α is the **temperature coefficient of resistivity**, defined as the fractional change in resistivity per unit rise in temperature:


$$\alpha = \frac{\rho - \rho_0}{\rho_0(T - T_0)} = \frac{1}{\rho_0}\frac{d\rho}{dT}$$

The SI unit of α is K^{-1} or $^\circ\text{C}^{-1}$.

Since the dimensions l and A change negligibly due to thermal expansion compared to the variation in ρ, resistance follows the identical temperature law:

$$R(T) = R_0[1 + \alpha(T - T_0)]$$

BOSONANCE

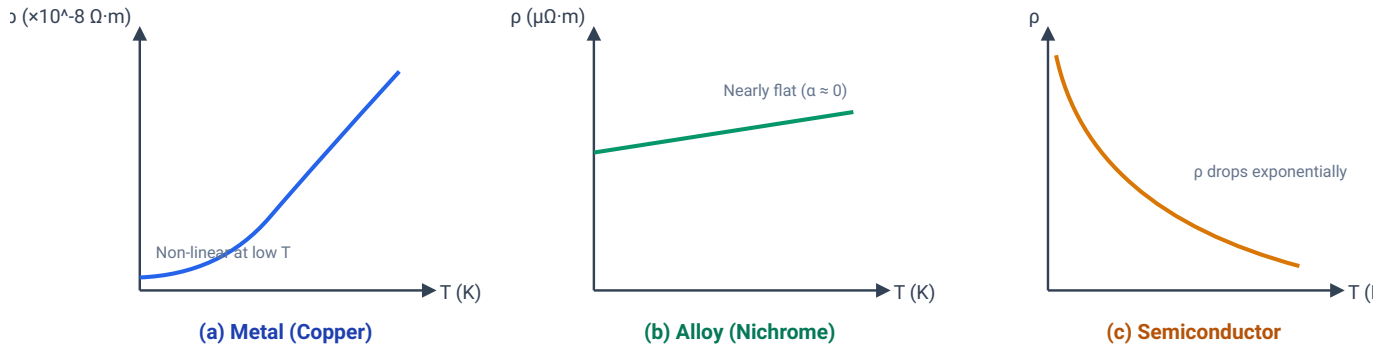

Tutorial Diagram 3: Temperature dependence of electrical resistivity $\rho(T)$ for (a) pure copper (non-linear below $50\,\mathrm{K}$), (b) nichrome alloy (high baseline, nearly independent of T), and (c) a typical semiconductor (exponential decrease, $\alpha < 0$).

5.2 Microscopic Explanation of Temperature Effects

Recall our derived microscopic relation for resistivity:

$$\rho = \frac{m}{ne^2\tau}$$

Resistivity is inversely proportional to both charge-carrier density n and mean relaxation time τ. The temperature dependence reflects a competition between these two microscopic factors:


Material Class	Carrier Density $n(T)$	Relaxation Time $\tau(T)$	Sign of α	Net Effect on Resistivity ρ
Metals (Conductors)	Constant (independent of T, $\sim 10^{29}\,\mathrm{m}^{-3}$)	Decreases significantly due to increased amplitude of ion vibrations and collision frequency	**Positive** ($\alpha > 0$)	Resistivity increases with temperature. (At very low temperatures $T \to 0\,\mathrm{K}$, ρ levels off to a residual value).
Standard Alloys (Nichrome, Manganin, Constantan)	Nearly constant	Scattering is dominated by structural disorder and impurity sites rather than thermal phonons	**Extremely small positive** ($\alpha \approx 10^{-5}\,\mathrm{K}^{-1}$)	High baseline resistivity that changes negligibly with temperature. Ideal for wire-wound standard resistors and heating elements.
Semiconductors & Insulators	Increases exponentially with T as covalent bonds break: $n(T) \propto e^{-E_g/(2k_\mathrm{B}T)}$	Decreases slightly due to increased scattering	**Negative** ($\alpha < 0$)	The dramatic exponential growth in n overwhelmingly dominates over the decrease in τ, causing resistivity to fall sharply.

6. Limitations of Ohm's Law and Non-Ohmic Devices

Ohm's law is a useful empirical relationship obeyed by many materials under controlled conditions, but it is **not a fundamental law of nature** (unlike Gauss's Law or Coulomb's Law). The equation $R = V/I$ serves merely as the operational definition of resistance for any device; Ohm's law asserts specifically that R *is a constant, independent of the applied voltage* V *or current magnitude and polarity*.

Materials and electronic devices that do not obey this strict linear proportionality are classified as **non-Ohmic devices**. Departures fall into three primary categories:

BOSONANCE

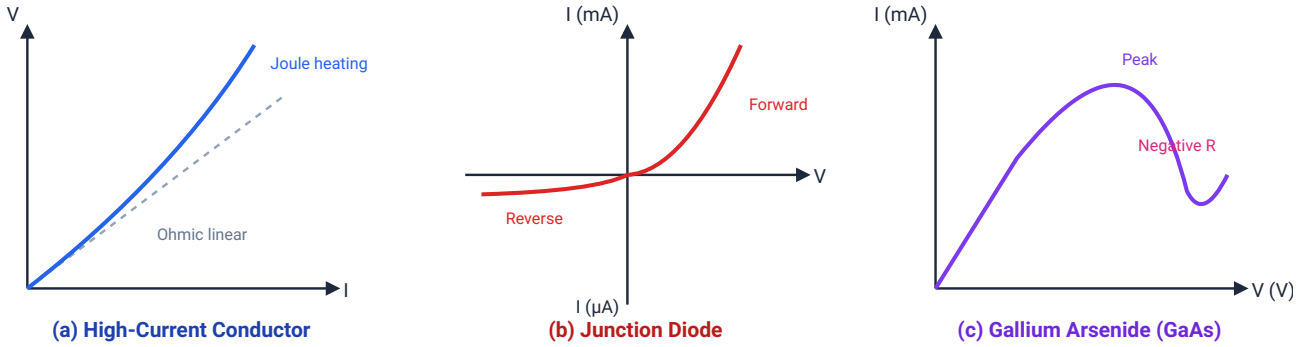

Tutorial Diagram 4: Non-Ohmic $V - I$ characteristic curves: (a) Metallic conductor deviating from linearity at high currents due to Joule heating, (b) Semiconductor junction diode demonstrating polarity-dependent rectification, and (c) Gallium Arsenide (GaAs) exhibiting a non-linear region, threshold peak, and negative differential resistance region ($dI/dV < 0$).

5.3 Classification of Non-Ohmic Behaviors

1. **Non-Linearity without Polarity Sensitivity:** In standard incandescent metallic lamp filaments, high currents cause severe Joule heating, increasing resistance. Consequently, V increases faster than I, bending the curve away from the linear Ohmic dashed line.
2. **Polarity Dependence (Rectification):** In semiconductor p-n junction diodes, reversing the polarity of the applied voltage V at fixed magnitude does not produce a current of identical magnitude in the opposite direction. A forward bias voltage of $\approx 0.7\,\mathrm{V}$ drives currents of several milliamperes (mA), whereas reverse bias allows only microamperes ($\mu\mathrm{A}$) until breakdown occurs.
3. **Non-Unique $V - I$ Relation (Negative Differential Resistance):** In advanced materials like **Gallium Arsenide (GaAs)** or tunnel diodes, the relation between current and voltage is not monotonic. For a single value of current I, multiple distinct operating voltages V exist. In the region where current decreases as voltage increases, the **dynamic resistance** is negative:

$$r_{\text{dynamic}} = \frac{\Delta V}{\Delta I} < 0$$

7. Electrical Energy, Power, and High-Voltage Power Transmission

7.1 Work Done by Electric Field and Joule's Law

Consider a conductor carrying steady current I from terminal A to terminal B, with potential difference $V = V_{\mathrm{A}} - V_{\mathrm{B}} > 0$. In time interval Δt, an amount of charge $\Delta Q = I\Delta t$ moves from A to B. The change in electrostatic potential energy is:

$$\Delta U = \Delta Q[V_{\mathrm{B}} - V_{\mathrm{A}}] = -\Delta Q\, V = -IV\Delta t < 0$$

If charges traveled through empty space without resistance, this lost potential energy would convert purely into macroscopic kinetic energy ($\Delta K = -\Delta U$). However, inside a real conductor, electrons undergo repeated collisions with lattice ions, transferring their gained kinetic energy to the lattice. The ions vibrate more vigorously, dissipating energy as thermal heat. The total heat energy ΔW released in the conductor in time Δt is:

$$\Delta W = IV\Delta t$$

The rate of electrical energy dissipation is the **electric power** P:

BOSONANCE

$$P = \frac{\Delta W}{\Delta t} = IV$$

Using Ohm's law ($V = IR$ and $I = V/R$), we obtain the classic equivalent formulations for Ohmic power loss:

$$P = IV = I^2R = \frac{V^2}{R}$$

7.2 Physics of High-Voltage Electric Power Transmission

Generating stations (hydroelectric, thermal, or nuclear) are typically situated hundreds of kilometres away from populated towns and industrial centres. Electrical energy must be transmitted across long distances using transmission lines with unavoidable total resistance R_c.

Suppose electrical power P is to be delivered to a city substation at voltage V. The transmission line current is:

$$I = \frac{P}{V}$$

The power wasted as Joule heat in the transmission lines (line loss, P_c) is:

$$P_c = I^2R_c = \left(\frac{P}{V}\right)^2 R_c = \frac{P^2R_c}{V^2}$$

Crucial NEET Deduction: Transmission Loss is Inversely Proportional to V^2

For a fixed transmitted power P and fixed line resistance R_c, the power lost in the cables is **inversely proportional to the square of the transmission voltage** ($P_c \propto 1/V^2$).

Example: Stepping up the transmission voltage by a factor of 10 reduces the wasted line power by a factor of $10^2 = 100$. This explains why long-distance overhead transmission cables operate at enormous potential differences (such as $132\,\text{kV}$, $220\,\text{kV}$, or $400\,\text{kV}$), requiring step-down transformers at destination substations for safe domestic use ($230\,\text{V}$).

BOSONANCE

8. Electrochemical Cells, EMF, and Internal Resistance

8.1 Electromotive Force (EMF) and Internal Resistance

A simple electrolytic cell consists of two conducting electrodes—a positive plate (P) and a negative plate (N)—immersed in an electrolytic solution. Due to chemical redox affinities:


- Electrode P establishes a positive potential V_+ ($V_+ > 0$) relative to the electrolyte immediately adjacent to it.
- Electrode N establishes a negative potential $-V_-$ ($V_- \geq 0$) relative to the electrolyte adjacent to it.

In an **open circuit** (when no current is drawn, $I = 0$), the electrolyte has uniform electric potential throughout. The net potential difference between P and N is called the **electromotive force (ε)** of the cell:

$$\varepsilon = V_+ - (-V_-) = V_+ + V_- > 0$$

Clarification: EMF is Not a Force

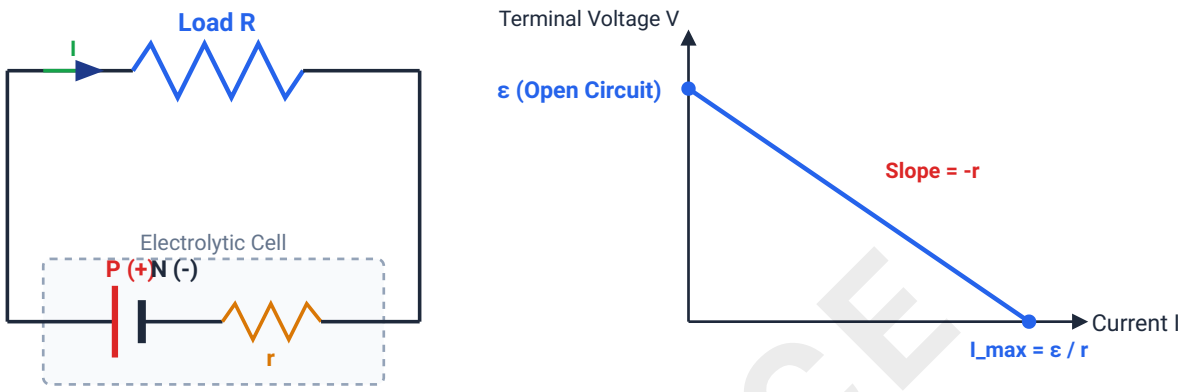Despite its historical name, electromotive force is **not a mechanical force** (its SI unit is the **volt**, not the newton). Rather, it represents the **work done per unit charge by non-electrostatic chemical forces** in transporting a positive charge from the negative terminal to the positive terminal inside the cell against the internal electric field.



Tutorial Diagram 5: Left: Closed circuit featuring an active cell of EMF ε and internal resistance r connected to load R. Right: Terminal voltage V plotted against load current I, intercepting $V = \varepsilon$ at $I = 0$ with negative slope $-r$.

8.2 Discharging vs. Charging Terminal Voltage

The electrolyte situated between plates P and N opposes the migration of ions, possessing a finite internal resistance r.


Operational Mode	Current Direction through Cell	Terminal Potential Difference (V)	Physical Significance
Open Circuit	$I = 0$	$V = \varepsilon$	No current flows; terminal voltage equals the full open-circuit EMF.
Discharging (Delivering Power)	Leaves positive plate P, enters negative plate N (flows $\mathrm{N} \to \mathrm{P}$ internally)	$V = \varepsilon - Ir < \varepsilon$	Internal resistance consumes voltage drop Ir; terminal voltage drops below ε.
Charging (Absorbing Power)	Driven into positive plate P by external source (flows $\mathrm{P} \to \mathrm{N}$ internally)	$V = \varepsilon + Ir > \varepsilon$	External charging source must overcome both the cell EMF and internal drop Ir.
Short Circuit	$R = 0$	$V = 0 \implies I_{\max} = \frac{\varepsilon}{r}$	Maximum possible discharge current drawn; all voltage drops across internal resistance r.

9. Grouping and Combinations of Cells

9.1 Cells in Series Combination

Consider two cells of EMFs $\varepsilon_1, \varepsilon_2$ and internal resistances r_1, r_2 connected in series across external terminals A and C:

BOSONANCE

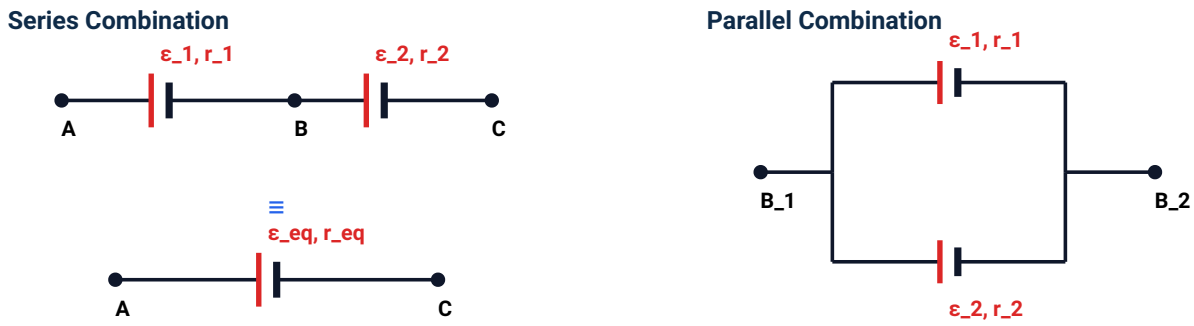

Tutorial Diagram 6: Grouping of cells. Left: Series grouping of two aiding cells. Right: Parallel combination of two distinct cells across junction nodes B_1 and B_2.

Let current I leave terminal A. The terminal potential differences are:

$$V_{\mathrm{AB}} = \varepsilon_1 - Ir_1 \quad \text{and} \quad V_{\mathrm{BC}} = \varepsilon_2 - Ir_2$$

Summing potential drops across the entire combination:

$$V_{\mathrm{AC}} = V_{\mathrm{AB}} + V_{\mathrm{BC}} = (\varepsilon_1 + \varepsilon_2) - I(r_1 + r_2)$$

Comparing this with an equivalent single cell $V_{\mathrm{AC}} = \varepsilon_{\mathrm{eq}} - Ir_{\mathrm{eq}}$ yields:

$$\varepsilon_{\mathrm{eq}} = \varepsilon_1 + \varepsilon_2 \quad \text{and} \quad r_{\mathrm{eq}} = r_1 + r_2$$

Opposing Polarity Rule: If cell 2 is reversed such that its positive plate connects to the positive plate of cell 1, then:

$$\varepsilon_{\mathrm{eq}} = \varepsilon_1 - \varepsilon_2 \quad (\text{assuming } \varepsilon_1 > \varepsilon_2) \quad \text{while} \quad r_{\mathrm{eq}} = r_1 + r_2$$

Note: Internal resistances always add arithmetically, regardless of battery orientation!

9.2 Cells in Parallel Combination

Let two cells (ε_1, r_1) and (ε_2, r_2) have their positive terminals connected to junction B_1 and negative terminals connected to junction B_2. The total current entering node B_1 is $I = I_1 + I_2$.

The potential difference $V = V(B_1) - V(B_2)$ is common across both branches:

$$V = \varepsilon_1 - I_1 r_1 \implies I_1 = \frac{\varepsilon_1 - V}{r_1}$$
$$V = \varepsilon_2 - I_2 r_2 \implies I_2 = \frac{\varepsilon_2 - V}{r_2}$$

Summing the branch currents:

BOSONANCE

$$I = I_1 + I_2 = \left(\frac{\varepsilon_1}{r_1} + \frac{\varepsilon_2}{r_2}\right) - V\left(\frac{1}{r_1} + \frac{1}{r_2}\right)$$

Rearranging for terminal voltage V:

$$V = \frac{\frac{\varepsilon_1}{r_1} + \frac{\varepsilon_2}{r_2}}{\frac{1}{r_1} + \frac{1}{r_2}} - I\left(\frac{1}{\frac{1}{r_1} + \frac{1}{r_2}}\right)$$

Equating this to $V = \varepsilon_{\text{eq}} - Ir_{\text{eq}}$ leads to the universal parallel cell equations:

$$\frac{1}{r_{\text{eq}}} = \frac{1}{r_1} + \frac{1}{r_2} \implies r_{\text{eq}} = \frac{r_1 r_2}{r_1 + r_2}$$
$$\frac{\varepsilon_{\text{eq}}}{r_{\text{eq}}} = \frac{\varepsilon_1}{r_1} + \frac{\varepsilon_2}{r_2} \implies \varepsilon_{\text{eq}} = \frac{\varepsilon_1 r_2 + \varepsilon_2 r_1}{r_1 + r_2}$$

NEET Special Case: Identical Cells in Parallel

If m identical cells (each with EMF ε and internal resistance r) are joined in parallel:

$$\varepsilon_{\text{eq}} = \varepsilon \quad \text{and} \quad r_{\text{eq}} = \frac{r}{m}$$

Conclusion: Connecting identical cells in parallel does not increase the EMF, but it reduces internal resistance by a factor of m, enabling high load currents without severe internal voltage drops.

10. Kirchhoff's Circuit Rules and Network Analysis

While series-parallel equivalence rules suffice for simple ladder circuits, complex multiloop networks require the systematic application of **Kirchhoff's Rules**, established by Gustav Robert Kirchhoff in 1845.

10.1 Kirchhoff's First Rule: The Junction Rule (KCL)

Statement: *At any junction (node) of an electrical network, the algebraic sum of currents meeting at that junction is zero. Equivalently, the sum of currents entering a junction equals the sum of currents leaving it.*

$$\sum I_{\text{in}} = \sum I_{\text{out}} \quad \text{or} \quad \sum_{k=1}^{n} I_k = 0$$

Fundamental Conservation Law Behind Junction Rule

The Junction Rule is a direct mathematical consequence of **the law of conservation of electric charge**. In steady-state DC conduction, electric charge cannot accumulate indefinitely or deplete at any point, junction, or cross-section. The rate of charge influx must strictly match the rate of charge efflux ($dq_{\text{in}}/dt = dq_{\text{out}}/dt$).

10.2 Kirchhoff's Second Rule: The Loop Rule (KVL)

Statement: *The algebraic sum of changes in potential encountered around any closed circuit loop involving resistors and cells is identically zero.*

BOSONANCE

$$\sum \Delta V = 0$$

Fundamental Conservation Law Behind Loop Rule


The Loop Rule is a direct consequence of **the law of conservation of energy** and the conservative nature of electrostatic fields. Since electric potential $V(\mathbf{r})$ is a single-valued scalar function of spatial position, tracing a closed loop and returning to the exact starting coordinate implies that the net change in potential energy of a test charge is zero ($\oint \mathbf{E} \cdot d\mathbf{l} = 0$).

10.3 Systematic Sign Conventions for Loop Traversal

1. **Traversing a Resistor:**
   - If you traverse a resistor in the *same direction* as the assigned branch current, you move from higher to lower potential: $\Delta V = -IR$.
   - If you traverse a resistor in the *opposite direction* to the assigned current, you move from lower to higher potential: $\Delta V = +IR$.

2. **Traversing an EMF Source (Cell):**
   - Traversing from negative terminal to positive terminal ($-$ to $+$) represents a potential rise: $\Delta V = +\varepsilon$.
   - Traversing from positive terminal to negative terminal ($+$ to $-$) represents a potential drop: $\Delta V = -\varepsilon$.
   - *(Note: The sign of ε depends exclusively on the cell terminal polarity traversed, regardless of the direction of current flowing through the cell!)*

BOSONANCE

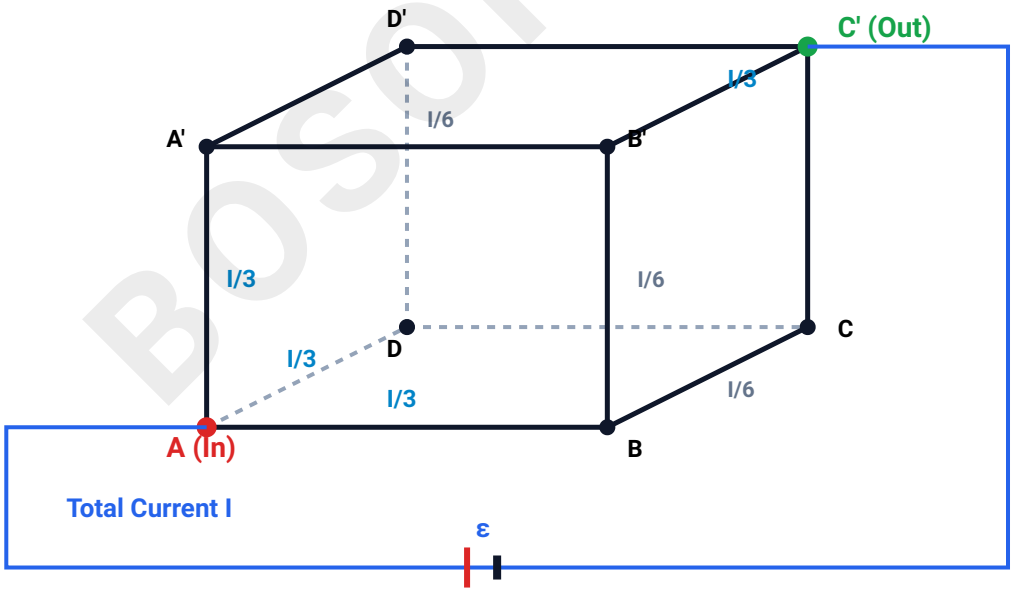

Tutorial Diagram 7: Cubical resistor network of 12 identical resistors (each of resistance R) connected across body diagonal opposite corners A and C'. Symmetry distributes input current I into three $I/3$ branches, each subsequently splitting into two $I/6$ branches.

11. The Wheatstone Bridge


11.1 Bridge Configuration

Devised by Samuel Hunter Christie and popularized by Sir Charles Wheatstone, the **Wheatstone bridge** is an elegant four-resistor network designed to measure unknown electrical resistances with outstanding precision via a null-deflection method.

The network comprises four resistive arms arranged as a closed quadrilateral ABCD:

- Arm AB: Resistance R_1
- Arm BC: Resistance R_2
- Arm AD: Resistance R_3
- Arm DC: Resistance R_4

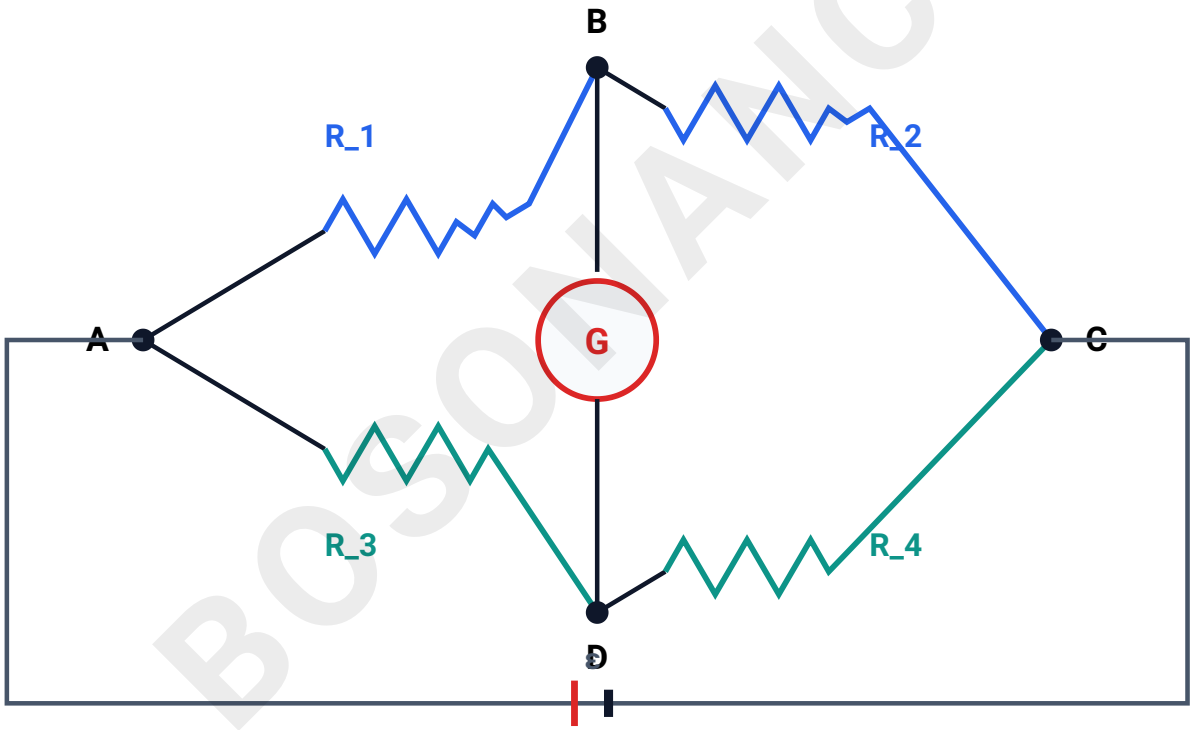Across diagonally opposite vertices A and C, an external EMF source ε is attached (called the **battery arm**). Across the remaining vertices B and D, a sensitive galvanometer G of internal resistance R_g is connected (called the **galvanometer arm**).



Tutorial Diagram 8: The Wheatstone Bridge arrangement. Four resistance arms R_1, R_2, R_3, R_4 with galvanometer G connected across BD and battery source ε connected across AC.

11.2 Derivation of the Balance Condition

A Wheatstone bridge is said to be **balanced** when the potential at vertex B equals the potential at vertex D ($V_{\mathrm{B}} = V_{\mathrm{D}}$). In this balanced state, the potential difference across the galvanometer is zero, so no current flows through it:

$$I_g = 0$$

Applying Kirchhoff's Junction Rule at node B and node D when $I_g = 0$:

$$I_{\text{AB}} = I_{\text{BC}} \implies I_1 = I_2$$
$$I_{\text{AD}} = I_{\text{DC}} \implies I_3 = I_4$$

Applying Kirchhoff's Loop Rule to closed loop ABDA in the clockwise direction:

$$-I_1R_1 - I_gR_g + I_3R_3 = 0 \implies I_1R_1 = I_3R_3 \implies \frac{I_1}{I_3} = \frac{R_3}{R_1} \qquad \text{(Eq. 1)}$$

Applying the Loop Rule to closed loop BCDB in the clockwise direction:

$$-I_2R_2 + I_4R_4 + I_gR_g = 0 \implies I_2R_2 = I_4R_4$$

Substituting $I_2 = I_1$ and $I_4 = I_3$:

$$I_1R_2 = I_3R_4 \implies \frac{I_1}{I_3} = \frac{R_4}{R_2} \qquad \text{(Eq. 2)}$$

Equating Eq. 1 and Eq. 2 gives the celebrated **Wheatstone Bridge Balance Condition**:

$$\frac{R_1}{R_2} = \frac{R_3}{R_4} \quad \text{or} \quad \frac{R_2}{R_1} = \frac{R_4}{R_3}$$

Three High-Yield NEET Properties of the Wheatstone Bridge

1. **Null Measurement Independence:** Because the measurement is executed at null deflection ($I_g = 0$), the internal resistance of the galvanometer and the internal resistance of the driver battery do not affect the balance condition!
2. **Conjugate Arms Theorem:** If the positions of the galvanometer and the battery are interchanged (i.e., battery connected across BD and galvanometer across AC), *the condition for null balance remains completely unchanged*. Arms AC and BD are called conjugate arms.
3. **Maximum Sensitivity Condition:** The bridge achieves its highest detection sensitivity when all four resistances are of roughly comparable magnitude ($R_1 \approx R_2 \approx R_3 \approx R_4$).

BOSONANCE

12. Comprehensive Worked Examples (NEET UG Standard)

Worked Example 1: Microscopic Drift Speed and Electron Transit Time

Problem: A uniform copper wire of length $3.0\,\text{m}$ and cross-sectional area $2.0 \times 10^{-6}\,\text{m}^2$ carries a steady current of $3.0\,\text{A}$. The conduction electron density of copper is $8.5 \times 10^{28}\,\text{m}^{-3}$. Calculate:
(a) The average drift speed of the conduction electrons.
(b) The time taken by an electron to drift from one end of the wire to the other.

Complete Worked Solution:

Part (a): Drift speed calculation:

Using the fundamental relation between electric current and drift speed:

$$I = neAv_d \implies v_d = \frac{I}{neA}$$

Substitute the given parameters: $I = 3.0\,\text{A}$, $n = 8.5 \times 10^{28}\,\text{m}^{-3}$, $e = 1.6 \times 10^{-19}\,\text{C}$, and $A = 2.0 \times 10^{-6}\,\text{m}^2$:

$$v_d = \frac{3.0}{(8.5 \times 10^{28}) \times (1.6 \times 10^{-19}) \times (2.0 \times 10^{-6})}$$

$$v_d = \frac{3.0}{2.72 \times 10^{4}} \approx 1.103 \times 10^{-4}\,\text{m}\,\text{s}^{-1} = 0.11\,\text{mm}\,\text{s}^{-1}$$

Part (b): Transit time calculation:

The time t required for an electron to traverse the length $l = 3.0\,\text{m}$ at this average drift speed is:

$$t = \frac{l}{v_d} = \frac{3.0\,\text{m}}{1.103 \times 10^{-4}\,\text{m}\,\text{s}^{-1}} \approx 2.72 \times 10^{4}\,\text{s}$$

Converting into hours:

$$t = \frac{27200}{3600}\,\text{hours} \approx 7.56\,\text{hours} \quad (\approx 7\,\text{hours and } 33\,\text{minutes})$$

Conclusion: Even though an electron takes over 7.5 hours to physically drift across a 3-metre wire, circuit response is instantaneous because the electric field establishes itself along the wire at $\approx 3 \times 10^{8}\,\text{m}\,\text{s}^{-1}$.

BOSONANCE

Worked Example 2: Wire Drawing and Percentage Resistance Variation

Problem: A cylindrical metallic wire having initial resistance $R = 10\,\Omega$ is drawn through a die such that its length increases uniformly by 20% of its initial length. Assuming the density and resistivity of the metal remain constant during the deformation, determine the new resistance of the wire.

Complete Worked Solution:

Let the initial length and cross-sectional area be l and A, and the final values be l' and A'.

The new length is:

$$l' = l + 0.20\,l = 1.20\,l$$

Because the volume of metal is conserved during drawing:

$$V = A \cdot l = A' \cdot l' \implies A' = A\left(\frac{l}{l'}\right) = \frac{A}{1.20}$$

The new resistance R' is:

$$R' = \rho\frac{l'}{A'} = \rho\frac{1.20\,l}{A/1.20} = (1.20)^2\left(\rho\frac{l}{A}\right) = 1.44\,R$$

Substituting $R = 10\,\Omega$:

$$R' = 1.44 \times 10\,\Omega = 14.4\,\Omega$$

Note: The fractional increase is $\Delta R/R = 44\%$. Note that the approximation $\Delta R/R \approx 2\Delta l/l$ yields 40%, which is invalid for large deformations like 20%. Always use the exact squared-ratio method for changes $> 5\%$.

Worked Example 3: Temperature Coefficient & Resistance Thermometry

Problem: The resistance of the platinum wire of a platinum resistance thermometer is found to be $5.00\,\Omega$ at the ice point ($0\,^\circ\mathrm{C}$) and $5.23\,\Omega$ at the steam point ($100\,^\circ\mathrm{C}$). When the thermometer is immersed in an unknown heated oil bath, the resistance is measured to be $5.795\,\Omega$. Calculate the temperature of the oil bath.

Complete Worked Solution:

We are given $R_0 = 5.00\,\Omega$ at $T_0 = 0\,^\circ\mathrm{C}$, and $R_{100} = 5.23\,\Omega$ at $T = 100\,^\circ\mathrm{C}$.

The temperature coefficient of resistance α is given by:

$$R_{100} = R_0[1 + \alpha(100 - 0)] \implies \alpha = \frac{R_{100} - R_0}{R_0 \times 100}$$

$$\alpha = \frac{5.23 - 5.00}{5.00 \times 100} = \frac{0.23}{500} = 4.60 \times 10^{-4}\,^\circ\mathrm{C}^{-1}$$

At the unknown oil bath temperature t:

$$R_t = R_0[1 + \alpha t] \implies t = \frac{R_t - R_0}{R_0\alpha}$$

Alternatively, expressing directly as a ratio:

$$t = \frac{R_t - R_0}{R_{100} - R_0} \times 100\,^\circ\mathrm{C}$$

$$t = \frac{5.795 - 5.000}{5.230 - 5.000} \times 100 = \frac{0.795}{0.230} \times 100 \approx 345.65\,^\circ\mathrm{C}$$

The temperature of the bath is $345.65\,^\circ\mathrm{C}$.

BOSONANCE

Worked Example 4: Battery Charging Circuit and Series Limiting Resistor

Problem: A secondary storage battery having an EMF of $8.0\,\text{V}$ and internal resistance of $0.5\,\Omega$ is being recharged from a $120\,\text{V}$ DC mains supply using an external series current-limiting resistor of $15.5\,\Omega$.
(a) Find the charging current flowing into the battery.
(b) Calculate the terminal voltage of the battery during charging.
(c) State the essential engineering purpose of including the $15.5\,\Omega$ series resistor.

Complete Worked Solution:

Part (a): Charging current:

During charging, the positive terminal of the DC charger is connected to the positive terminal of the battery, setting up an opposing EMF. The net driving EMF around the loop is:

$$\varepsilon_{\text{net}} = V_{\text{mains}} - \varepsilon_{\text{battery}} = 120\,\text{V} - 8.0\,\text{V} = 112\,\text{V}$$

The total resistance of the charging circuit is the sum of external and internal resistance:

$$R_{\text{total}} = R_{\text{series}} + r = 15.5\,\Omega + 0.5\,\Omega = 16.0\,\Omega$$

The charging current I is therefore:

$$I = \frac{\varepsilon_{\text{net}}}{R_{\text{total}}} = \frac{112\,\text{V}}{16.0\,\Omega} = 7.0\,\text{A}$$

Part (b): Terminal voltage during charging:

Because the cell is being charged (current forced into the positive plate):

$$V = \varepsilon + Ir = 8.0\,\text{V} + (7.0\,\text{A} \times 0.5\,\Omega) = 8.0\,\text{V} + 3.5\,\text{V} = 11.5\,\text{V}$$

Part (c): Role of the series resistor:

The battery's internal resistance is tiny ($0.5\,\Omega$). Without the series resistor, the charging current would skyrocket to $I = 112\,\text{V}/0.5\,\Omega = 224\,\text{A}$. This massive current would instantly boil the electrolyte, buckle the electrode plates, and destroy the battery. The series resistor safely limits the current to a manageable $7.0\,\text{A}$.

BOSONANCE

Worked Example 5: Non-Identical Cells in Parallel with Opposing Polarities

Problem: Two cells of EMF $\varepsilon_1 = 6.0\,\text{V}$ and $\varepsilon_2 = 4.0\,\text{V}$, having internal resistances $r_1 = 1.0\,\Omega$ and $r_2 = 2.0\,\Omega$ respectively, are connected in parallel. However, the positive terminal of cell 1 is connected to the negative terminal of cell 2. Find the equivalent EMF and equivalent internal resistance of the combination.

Complete Worked Solution:

The equivalent internal resistance of two parallel branches depends only on the resistances, unaffected by battery polarities:

$$\frac{1}{r_{\text{eq}}} = \frac{1}{r_1} + \frac{1}{r_2} = \frac{1}{1.0} + \frac{1}{2.0} = 1.5\,\Omega^{-1} \implies r_{\text{eq}} = \frac{1}{1.5} = \frac{2}{3}\,\Omega \approx 0.67\,\Omega$$

Because the cell polarities are connected in opposition, one EMF enters with a negative sign:

$$\frac{\varepsilon_{\text{eq}}}{r_{\text{eq}}} = \frac{\varepsilon_1}{r_1} - \frac{\varepsilon_2}{r_2}$$

$$\frac{\varepsilon_{\text{eq}}}{2/3} = \frac{6.0}{1.0} - \frac{4.0}{2.0} = 6.0 - 2.0 = 4.0\,\text{A}$$

$$\varepsilon_{\text{eq}} = 4.0 \times \frac{2}{3} = \frac{8}{3}\,\text{V} \approx 2.67\,\text{V}$$

The equivalent EMF is $2.67\,\text{V}$ (with polarity governed by cell 1), and the equivalent internal resistance is $0.67\,\Omega$.

BOSONANCE

Worked Example 6: Symmetrical Resistor Cube Across Body Diagonal

Problem: A network formed by 12 identical uniform resistors, each of resistance $R = 6\,\Omega$, forms the edges of a cube. A $10\,\mathrm{V}$ battery of negligible internal resistance is connected across diagonally opposite body corners of the cube. Find:
(a) The equivalent resistance of the entire cubical network.
(b) The total current supplied by the battery.
(c) The current flowing through each individual resistor edge.

Complete Worked Solution:

Part (a): Equivalent Resistance:

Let input corner be A and diagonally opposite exit corner be C'.

By three-fold rotational symmetry about body diagonal AC':

1. At input vertex A, current $I_{\text{total}} = 3I$ divides equally into three identical edge branches: each carries current I.
2. At each of the three secondary vertices, the current I encounters two identical departing edges, splitting equally into $I/2$.
3. At the three tertiary vertices, pairs of $I/2$ currents merge back into branches of current I heading toward exit corner C'.

Now, apply Kirchhoff's loop rule along any path from A to C' through the battery (such as path $\mathrm{A} \to \mathrm{B} \to \mathrm{C} \to \mathrm{C}' \to \text{battery} \to \mathrm{A}$):

$$\varepsilon - IR - \frac{1}{2}IR - IR = 0 \implies \varepsilon = \left(1 + \frac{1}{2} + 1\right)IR = \frac{5}{2}IR$$

Since the total current supplied by the source is $I_{\text{total}} = 3I$, the equivalent resistance R_{eq} is:

$$R_{\text{eq}} = \frac{\varepsilon}{I_{\text{total}}} = \frac{\frac{5}{2}IR}{3I} = \frac{5}{6}R$$

Given $R = 6\,\Omega$:

$$R_{\text{eq}} = \frac{5}{6} \times 6\,\Omega = 5\,\Omega$$

Part (b): Total Current:

$$I_{\text{total}} = \frac{\varepsilon}{R_{\text{eq}}} = \frac{10\,\mathrm{V}}{5\,\Omega} = 2.0\,\mathrm{A}$$

Part (c): Current along individual edges:

Since $I_{\text{total}} = 3I = 2.0\,\mathrm{A} \implies I = \frac{2.0}{3}\,\mathrm{A} \approx 0.67\,\mathrm{A}$:

- The 3 edges directly connected to input vertex A carry $I = 0.67\,\mathrm{A}$.
- The 3 edges directly connected to output vertex C' carry $I = 0.67\,\mathrm{A}$.
- The remaining 6 intermediate edges carry $I/2 = \frac{0.67}{2} = 0.33\,\mathrm{A}\ (1/3\,\mathrm{A})$.

13. NEET UG Exam-Style Practice Questions

The following 15 practice questions are specifically designed to match the current NEET UG testing pattern, comprising standard numerical MCQs, multi-statement evaluations, Assertion-Reason pairs, and matching lists. Complete step-by-step solutions are provided for each question.

BOSONANCE

Practice Question 1 (Numerical MCQ): Drift Velocity in a Non-Uniform Conductor

A non-uniform copper conductor of circular cross-section carries a steady current I. The diameter of the wire at section 1 is d_1 and at section 2 is $d_2 = 2d_1$. If v_1 and v_2 represent the mean drift speeds of conduction electrons at section 1 and section 2 respectively, the ratio v_1/v_2 is:

(A) $1 : 2$

(B) $2 : 1$

(C) $4 : 1$

(D) $1 : 4$

Correct Option: (C)

Explanation: Under steady-state conditions, electric charge cannot accumulate anywhere along the wire; therefore, the current I is constant across every cross-section:

$$I = neA_1v_1 = neA_2v_2 \implies v \propto \frac{1}{A} \propto \frac{1}{d^2}$$

$$\frac{v_1}{v_2} = \left(\frac{d_2}{d_1}\right)^2 = \left(\frac{2d_1}{d_1}\right)^2 = 4$$

Thus, $v_1/v_2 = 4 : 1$.

BOSONANCE

Practice Question 2 (Conceptual MCQ): Field Dependence of Drift Speed vs. Mobility

A steady potential difference V is applied across a uniform metallic wire of fixed length l and cross-sectional area A. If the applied voltage V is doubled while maintaining constant temperature, what happens to the electron drift speed v_d and electron mobility μ?

(A) Both v_d and μ are doubled.

(B) v_d is doubled, while μ remains unchanged.

(C) Both v_d and μ remain unchanged.

(D) v_d is halved, while μ is doubled.

Correct Option: (B)

Explanation: The applied electric field is $E = V/l$. When V is doubled, E doubles.

1. Drift speed is directly proportional to E:

$$v_d = \frac{eE\tau}{m} = \frac{eV\tau}{ml} \implies v_d \propto V$$

Hence, doubling V doubles the drift speed v_d.

2. Mobility is defined as drift speed per unit field:

$$\mu = \frac{v_d}{E} = \frac{e\tau}{m}$$

Since the relaxation time τ and electron mass m depend on temperature and material properties (which are held constant), mobility μ is **independent of the applied electric field E and voltage V**.

BOSONANCE

Practice Question 3 (Numerical MCQ): Mass and Length Ratios in Resistor Wires

Three copper wires have their masses in the ratio $1:3:5$ and their lengths in the ratio $5:3:1$. The ratio of their electrical resistances $R_1:R_2:R_3$ is:

(A) $1:3:5$

(B) $5:3:1$

(C) $1:15:125$

(D) $125:15:1$

Correct Option: (D)

Explanation: The mass of a wire of length l, cross-sectional area A, and density d is $M = A \cdot l \cdot d \implies A = \frac{M}{ld}$.

The resistance of the wire is:

$$R = \rho\frac{l}{A} = \rho\frac{l}{M/(ld)} = \left(\frac{\rho d}{1}\right)\frac{l^2}{M} \implies R \propto \frac{l^2}{M}$$

Now evaluate the ratios:

$$R_1:R_2:R_3 = \frac{l_1^2}{M_1}:\frac{l_2^2}{M_2}:\frac{l_3^2}{M_3} = \frac{5^2}{1}:\frac{3^2}{3}:\frac{1^2}{5} = 25:3:\frac{1}{5}$$

Multiplying the entire ratio by 5 to clear the fraction:

$$R_1:R_2:R_3 = (25\times5):(3\times5):1 = 125:15:1$$

BOSONANCE

Practice Question 4 (Numerical MCQ): Temperature of a Nichrome Element

A heating element made of nichrome wire has a resistance of $80.0\,\Omega$ at room temperature ($27.0\,^\circ\mathrm{C}$). When connected to a $220\,\mathrm{V}$ DC supply, it draws a steady operating current of $2.5\,\mathrm{A}$. If the temperature coefficient of resistance of nichrome averaged over this range is $1.70 \times 10^{-4}\,^\circ\mathrm{C}^{-1}$, the steady operating temperature of the element is closest to:

(A) $588\,^\circ\mathrm{C}$

(B) $615\,^\circ\mathrm{C}$

(C) $847\,^\circ\mathrm{C}$

(D) $742\,^\circ\mathrm{C}$

Correct Option: (B)

Explanation: Initial resistance at $T_1 = 27.0\,^\circ\mathrm{C}$ is $R_1 = 80.0\,\Omega$.

The steady operating resistance R_2 at operating temperature T_2 is:

$$R_2 = \frac{V}{I} = \frac{220\,\mathrm{V}}{2.5\,\mathrm{A}} = 88.0\,\Omega$$

Using the temperature-resistance equation:

$$R_2 = R_1[1 + \alpha(T_2 - T_1)] \implies T_2 - T_1 = \frac{R_2 - R_1}{R_1 \alpha}$$

$$T_2 - 27.0 = \frac{88.0 - 80.0}{80.0 \times (1.70 \times 10^{-4})} = \frac{8.0}{0.0136} \approx 588.2\,^\circ\mathrm{C}$$

$$T_2 = 588.2 + 27.0 = 615.2\,^\circ\mathrm{C} \approx 615\,^\circ\mathrm{C}$$

BOSONANCE

Practice Question 5 (Assertion-Reason): Temperature Coefficients of Metals vs. Semiconductors

Assertion (A): The electrical resistivity of a semiconductor decreases exponentially with an increase in temperature, whereas that of a metallic conductor increases.

Reason (R): In metals, the free electron density is virtually independent of temperature and the collision frequency increases with temperature; in semiconductors, the exponential generation of electron-hole pairs overwhelmingly compensates for the decrease in relaxation time.

(A) Both (A) and (R) are true, and (R) is the correct explanation of (A).

(B) Both (A) and (R) are true, but (R) is NOT the correct explanation of (A).

(C) (A) is true, but (R) is false.

(D) Both (A) and (R) are false.

Correct Option: (A)

Explanation: From the microscopic relation $\rho = m/(ne^2\tau)$:

- For metals, n is fixed by metallic bonding ($\approx 10^{29}\ \mathrm{m}^{-3}$). As T rises, thermal lattice vibrations scatter electrons more frequently, reducing τ. Hence ρ increases ($\alpha > 0$).
- For semiconductors, thermal energy breaks covalent bonds, causing carrier density n to increase exponentially according to $n \propto e^{-E_g/(2k_\mathrm{B}T)}$. This exponential surge in n completely overwhelms the moderate decrease in τ, driving ρ downward ($\alpha < 0$). Both statements are scientifically accurate and (R) provides the complete microscopic rationale.

BOSONANCE

Practice Question 6 (Statement-Based MCQ): Non-Ohmic Conduction Phenomena

Consider the following two statements regarding electrical conduction:

Statement I: Ohm's law is a fundamental law of physics obeyed by all electrical conductors without exception.

Statement II: Gallium Arsenide (GaAs) exhibits a non-linear region followed by a region where dynamic resistance dV/dI is negative.

(A) Statement I is correct, but Statement II is incorrect.

(B) Statement I is incorrect, but Statement II is correct.

(C) Both Statement I and Statement II are correct.

(D) Both Statement I and Statement II are incorrect.

Correct Option: (B)

Explanation:

- **Statement I is incorrect:** Ohm's law is an empirical material relationship, not a universal fundamental law. Devices like p-n junction diodes, vacuum tubes, thyristors, and electrolytes deviate markedly from Ohm's law.
- **Statement II is correct:** Gallium Arsenide (GaAs) displays transferred-electron behavior (Gunn effect), producing a characteristic $V - I$ curve where current drops as voltage increases beyond a threshold, resulting in negative differential resistance.

BOSONANCE

Practice Question 7 (Numerical MCQ): Transmission Voltage and Line Loss Reduction

Electric power P is transmitted from a distant generating plant to a town through transmission lines having a total series resistance R_c. If the transmission voltage is increased from $11\,\mathrm{kV}$ to $110\,\mathrm{kV}$ to transmit the identical electrical power, the power dissipated as Joule heat in the transmission lines will:

(A) Increase by a factor of 10

(B) Decrease by a factor of 10

(C) Decrease by a factor of 100

(D) Remain unchanged

Correct Option: (C)

Explanation: For delivered power P at transmission voltage V, the transmission current is $I = P/V$. The power loss in the lines is:

$$P_c = I^2 R_c = \frac{P^2 R_c}{V^2} \implies P_c \propto \frac{1}{V^2}$$

Taking the ratio:

$$\frac{P_{c2}}{P_{c1}} = \left(\frac{V_1}{V_2}\right)^2 = \left(\frac{11\,\mathrm{kV}}{110\,\mathrm{kV}}\right)^2 = \left(\frac{1}{10}\right)^2 = \frac{1}{100}$$

Line power loss decreases by a factor of 100.

Practice Question 8 (Numerical MCQ): Active Terminal Voltage of a Discharging Battery

A battery of EMF $10.0\,\mathrm{V}$ and internal resistance $3.0\,\Omega$ is connected across an external resistor R. If the steady current flowing through the circuit is $0.50\,\mathrm{A}$, the resistance of resistor R and the terminal potential difference V across the battery are:

(A) $R = 17.0\,\Omega,\ V = 8.5\,\mathrm{V}$

(B) $R = 20.0\,\Omega,\ V = 10.0\,\mathrm{V}$

(C) $R = 17.0\,\Omega,\ V = 1.5\,\mathrm{V}$

(D) $R = 14.0\,\Omega,\ V = 7.0\,\mathrm{V}$

Correct Option: (A)

Explanation: The current in a simple closed single-loop circuit is:

$$I = \frac{\varepsilon}{R + r} \implies R + r = \frac{\varepsilon}{I} = \frac{10.0\,\mathrm{V}}{0.50\,\mathrm{A}} = 20.0\,\Omega$$

$$R = 20.0\,\Omega - r = 20.0\,\Omega - 3.0\,\Omega = 17.0\,\Omega$$

The terminal voltage V during discharge is:

$$V = \varepsilon - Ir = 10.0\,\mathrm{V} - (0.50\,\mathrm{A} \times 3.0\,\Omega) = 10.0\,\mathrm{V} - 1.5\,\mathrm{V} = 8.5\,\mathrm{V}$$

Equivalently, across the external load: $V = IR = 0.50 \times 17.0 = 8.5\,\mathrm{V}$.

BOSONANCE

Practice Question 9 (Numerical MCQ): Equivalent EMF of Parallel Cells

Two galvanic cells of EMF $\varepsilon_1 = 2.0\,\mathrm{V}$ and $\varepsilon_2 = 1.0\,\mathrm{V}$ have internal resistances $r_1 = 1.0\,\Omega$ and $r_2 = 2.0\,\Omega$ respectively. If their positive terminals are connected together and their negative terminals are connected together, the equivalent EMF $\varepsilon_{\mathrm{eq}}$ and internal resistance r_{eq} of the combination are:

(A) $\varepsilon_{\mathrm{eq}} = 1.5\,\mathrm{V},\ r_{\mathrm{eq}} = 3.0\,\Omega$

(B) $\varepsilon_{\mathrm{eq}} = 1.67\,\mathrm{V},\ r_{\mathrm{eq}} = 0.67\,\Omega$

(C) $\varepsilon_{\mathrm{eq}} = 3.0\,\mathrm{V},\ r_{\mathrm{eq}} = 0.67\,\Omega$

(D) $\varepsilon_{\mathrm{eq}} = 1.33\,\mathrm{V},\ r_{\mathrm{eq}} = 1.5\,\Omega$

Correct Option: (B)

Explanation: Using the parallel grouping formulas:

$$r_{\mathrm{eq}} = \frac{r_1 r_2}{r_1 + r_2} = \frac{1.0 \times 2.0}{1.0 + 2.0} = \frac{2}{3}\,\Omega \approx 0.67\,\Omega$$

$$\varepsilon_{\mathrm{eq}} = \frac{\varepsilon_1 r_2 + \varepsilon_2 r_1}{r_1 + r_2} = \frac{(2.0 \times 2.0) + (1.0 \times 1.0)}{1.0 + 2.0} = \frac{4.0 + 1.0}{3} = \frac{5}{3}\,\mathrm{V} \approx 1.67\,\mathrm{V}$$

Practice Question 10 (Matching List MCQ): Electrical Quantities, Formulas, and Units

Match the physical quantities in **Column I** with their correct mathematical formulations/SI units in **Column II**:

Column I (Quantity)	Column II (Expression / Unit)
P. Electrical Conductivity (σ)	1. $\frac{e\tau}{m}$ / $\mathrm{m^2\,V^{-1}\,s^{-1}}$
Q. Current Density ($\mathbf{j}$)	2. $\frac{m}{ne^2\tau}$ / $\Omega\,\mathrm{m}$
R. Carrier Mobility (μ)	3. $\frac{ne^2\tau}{m}$ / $\mathrm{S\,m^{-1}}$
S. Electrical Resistivity (ρ)	4. $ne\mathbf{v}_d$ / $\mathrm{A\,m^{-2}}$

(A) P-3, Q-4, R-1, S-2

(B) P-2, Q-1, R-4, S-3

(C) P-3, Q-1, R-4, S-2

(D) P-2, Q-4, R-1, S-3

Correct Option: (A)

Explanation:

- **P:** Conductivity $\sigma = \frac{ne^2\tau}{m}$, measured in $\mathrm{S\,m^{-1}}$ (matches 3).
- **Q:** Current density $\mathbf{j} = ne\mathbf{v}_d$, measured in $\mathrm{A\,m^{-2}}$ (matches 4).
- **R:** Mobility $\mu = \frac{v_d}{E} = \frac{e\tau}{m}$, measured in $\mathrm{m^2\,V^{-1}\,s^{-1}}$ (matches 1).
- **S:** Resistivity $\rho = \frac{m}{ne^2\tau}$, measured in $\Omega\,\mathrm{m}$ (matches 2).

BOSONANCE

Practice Question 11 (Conceptual MCQ): Conservation Principles in Kirchhoff's Laws

Kirchhoff's First Rule ($\sum I = 0$ at a junction) and Kirchhoff's Second Rule ($\sum \Delta V = 0$ around a closed loop) are respectively based on the fundamental laws of conservation of:

(A) Energy and Electric Charge

(B) Electric Charge and Momentum

(C) Electric Charge and Energy

(D) Momentum and Energy

Correct Option: (C)

Explanation:

- The Junction Rule equates the rate of charge entering a junction to the rate leaving it, reflecting **conservation of electric charge**.
- The Loop Rule states that the net work done in moving a test charge around any closed path in an electrostatic field is zero, reflecting **conservation of energy**.

Practice Question 12 (Numerical MCQ): Maximum Current from a Storage Cell

A storage battery of a motor vehicle has an EMF of $12.0\,\text{V}$ and an internal resistance of $0.40\,\Omega$. What is the theoretical maximum instantaneous current that can be drawn from this battery?

(A) $4.8\,\text{A}$

(B) $12.0\,\text{A}$

(C) $30.0\,\text{A}$

(D) $60.0\,\text{A}$

Correct Option: (C)

Explanation: The current delivered to an external load R is $I = \frac{\varepsilon}{R+r}$. The current achieves its absolute maximum when the external resistance is short-circuited ($R = 0$):

$$I_{\text{max}} = \frac{\varepsilon}{r} = \frac{12.0\,\text{V}}{0.40\,\Omega} = 30.0\,\text{A}$$

BOSONANCE

Practice Question 13 (Numerical MCQ): Unbalanced Wheatstone Bridge Branch Analysis

In a Wheatstone bridge network ABCD, the four arms have resistances: $R_{\mathrm{AB}} = 100\,\Omega$, $R_{\mathrm{BC}} = 10\,\Omega$, $R_{\mathrm{CD}} = 5\,\Omega$, and $R_{\mathrm{DA}} = 60\,\Omega$. A galvanometer of resistance $15\,\Omega$ is connected between B and D. If a potential difference of $10\,\mathrm{V}$ is maintained across AC, the current I_g through the galvanometer is approximately:

(A) $0.00\,\mathrm{mA}$

(B) $4.87\,\mathrm{mA}$

(C) $12.5\,\mathrm{mA}$

(D) $24.2\,\mathrm{mA}$

Correct Option: (B)

Explanation: Test balance condition first: $\frac{R_{\mathrm{AB}}}{R_{\mathrm{BC}}} = \frac{100}{10} = 10$; $\frac{R_{\mathrm{DA}}}{R_{\mathrm{CD}}} = \frac{60}{5} = 12$. Since $10 \neq 12$, the bridge is unbalanced and $I_g \neq 0$.

Applying Kirchhoff's loop rule to mesh BADB: $100I_1 + 15I_g - 60I_2 = 0 \implies 20I_1 + 3I_g - 12I_2 = 0$.

Applying to mesh BCDB: $10(I_1 - I_g) - 15I_g - 5(I_2 + I_g) = 0 \implies 2I_1 - 6I_g - I_2 = 0$.

Applying to loop ADCEA: $60I_2 + 5(I_2 + I_g) = 10 \implies 13I_2 + I_g = 2$.

Solving these three simultaneous equations:

$$I_2 = 31.5I_g \implies 13(31.5I_g) + I_g = 2 \implies 410.5I_g = 2$$

$$I_g = \frac{2}{410.5} \approx 4.87 \times 10^{-3}\,\mathrm{A} = 4.87\,\mathrm{mA}$$

BOSONANCE

Practice Question 14 (Assertion-Reason): Conjugate Arms of a Wheatstone Bridge

Assertion (A): If the positions of the galvanometer and the battery in a balanced Wheatstone bridge are interchanged, the galvanometer continues to show zero deflection.

Reason (R): The balance condition for a Wheatstone bridge depends on the ratio of adjacent resistances, which remains mathematically invariant under the interchange of the battery and galvanometer arms.

(A) Both (A) and (R) are true, and (R) is the correct explanation of (A).

(B) Both (A) and (R) are true, but (R) is NOT the correct explanation of (A).

(C) (A) is true, but (R) is false.

(D) (A) is false, but (R) is true.

Correct Option: (A)

Explanation: The initial balance condition is $\frac{R_1}{R_2} = \frac{R_3}{R_4}$, which cross-multiplies to $R_1R_4 = R_2R_3$. When the battery (initially across AC) and galvanometer (initially across BD) are interchanged, the bridge arms configure such that the new null condition is $\frac{R_1}{R_3} = \frac{R_2}{R_4}$. Cross-multiplying yields the identical product relation $R_1R_4 = R_2R_3$. Hence, both statements are correct and (R) correctly explains (A).

BOSONANCE

Practice Question 15 (Statement-Based MCQ): Vector Nature of Current Density & Ohm's Law

Evaluate the correctness of the following two statements:

Statement I: Electric current is a scalar quantity, but current density is a vector quantity pointing in the direction of the local electric field.

Statement II: The microscopic statement of Ohm's law, $\mathbf{j} = \sigma \mathbf{E}$, implies that the conductivity σ of an isotropic Ohmic medium is independent of both the magnitude and direction of the applied electric field.

(A) Statement I is correct, but Statement II is incorrect.

(B) Statement I is incorrect, but Statement II is correct.

(C) Both Statement I and Statement II are correct.

(D) Both Statement I and Statement II are incorrect.

Correct Option: (C)

Explanation:

- **Statement I is correct:** Current is a scalar (defined via surface flux $I = \int \mathbf{j} \cdot d\mathbf{S}$), whereas current density $\mathbf{j}$ has both magnitude ($dI/dS_\perp$) and direction along $\mathbf{E}$.
- **Statement II is correct:** A material obeys Ohm's law if and only if its conductivity σ (and resistivity ρ) is a constant independent of the applied electric field $\mathbf{E}$.

BOSONANCE

14. Common Pitfalls, NEET Traps & Exam Checklist

Frequent NEET Traps & How to Avoid Them

- **Trap 1: Confusing Drift Speed with Signal Velocity.** Remember that electrons drift sluggishly at $\approx 1\,\text{mm}\,\text{s}^{-1}$, while the electromagnetic signal establishes at $\approx 3 \times 10^8\,\text{m}\,\text{s}^{-1}$. Never calculate signal propagation time using v_d!
- **Trap 2: Wire Stretching Percentage Calculations.** If a wire is stretched by $n\%$ where $n \leq 5\%$, use $\Delta R/R \approx 2n\%$. However, if $n > 5\%$ (e.g., 20% or 100%), you *must* use the quadratic factor $R' = (1 + n/100)^2 R$. Using the linear formula for large stretching leads to wrong answer choices!
- **Trap 3: Battery Terminal Voltage Sign.** When a cell is *discharging*, $V = \varepsilon - Ir < \varepsilon$. When a cell is being *charged* by an external DC supply, $V = \varepsilon + Ir > \varepsilon$. Pay close attention to whether the problem states current is leaving or entering the positive terminal.
- **Trap 4: Internal Resistance of Cells in Opposing Series.** When two cells are connected in series with opposing polarities, their equivalent EMF is subtracted ($\varepsilon_{\text{eq}} = \varepsilon_1 - \varepsilon_2$), but their internal resistances **always add** ($r_{\text{eq}} = r_1 + r_2$). Never subtract resistances!
- **Trap 5: Definition of Ohm's Law.** Stating that $V = IR$ is Ohm's law is inaccurate; $V = IR$ merely defines resistance. Ohm's law specifically states that R is a constant independent of V and I.

Rapid Revision Checklist Before Entering the Exam Hall

- ☑ **Current Density:** $I = \mathbf{j} \cdot \mathbf{A} = jA\cos\theta$ (scalar), $\mathbf{j}$ is a vector in $\mathrm{A\,m^{-2}}$.
- ☑ **Drift Velocity:** $v_d = \frac{eE\tau}{m} = \frac{eV\tau}{ml}$; Current relation: $I = neAv_d$.
- ☑ **Mobility:** $\mu = \frac{v_d}{E} = \frac{e\tau}{m}$; strictly positive; unit $\mathrm{m^2\,V^{-1}\,s^{-1}}$.
- ☑ **Resistivity & Conductivity:** $\rho = \frac{m}{ne^2\tau}$, $\sigma = \frac{ne^2\tau}{m}$.
- ☑ **Temperature Dependence:** $\rho(T) = \rho_0[1 + \alpha(T - T_0)]$. Metals have $\alpha > 0$; semiconductors have $\alpha < 0$; standard alloys have $\alpha \approx 0$.
- ☑ **Power & Line Loss:** $P = VI = I^2R = V^2/R$; line loss $P_c = P^2R_c/V^2 \propto 1/V^2$.
- ☑ **Cell Discharging:** $V = \varepsilon - Ir$; **Charging:** $V = \varepsilon + Ir$; **Short circuit:** $I_{\max} = \varepsilon/r$.
- ☑ **Parallel Cells:** $\frac{\varepsilon_{\text{eq}}}{r_{\text{eq}}} = \frac{\varepsilon_1}{r_1} + \frac{\varepsilon_2}{r_2}$ and $\frac{1}{r_{\text{eq}}} = \frac{1}{r_1} + \frac{1}{r_2}$.
- ☑ **Kirchhoff's Rules:** Junction Rule $\rightarrow$ Charge conservation; Loop Rule $\rightarrow$ Energy conservation.
- ☑ **Wheatstone Bridge:** Balanced when $\frac{R_1}{R_2} = \frac{R_3}{R_4}$ ($I_g = 0$). Conjugate arms theorem permits swapping galvanometer and battery.

15. Master Formula Cheat-Sheet & Dimensional Review

Physical Quantity	Standard Symbol	Defining Equation	SI Unit	Dimensional Formula
Electric Current	I	$I = \frac{dQ}{dt} = neAv_d$	A (ampere)	$[\mathrm{M^0L^0T^0A^1}]$
Current Density	$\mathbf{j}$	$\mathbf{j} = \sigma\mathbf{E} = ne\mathbf{v}_d$	$\mathrm{A\,m^{-2}}$	$[\mathrm{M^0L^{-2}T^0A^1}]$
Drift Speed	v_d	$v_d = \frac{eE\tau}{m} = \frac{I}{neA}$	$\mathrm{m\,s^{-1}}$	$[\mathrm{M^0L^1T^{-1}A^0}]$
Electron Mobility	μ	$\mu = \frac{v_d}{E} = \frac{e\tau}{m}$	$\mathrm{m^2\,V^{-1}\,s^{-1}}$	$[\mathrm{M^{-1}L^0T^2A^1}]$
Electrical Resistance	R	$R = \frac{V}{I} = \rho\frac{l}{A}$	Ω (ohm)	$[\mathrm{M^1L^2T^{-3}A^{-2}}]$
Electrical Resistivity	ρ	$\rho = \frac{m}{ne^2\tau} = \frac{E}{j}$	$\Omega\,\mathrm{m}$	$[\mathrm{M^1L^3T^{-3}A^{-2}}]$
Electrical Conductivity	σ	$\sigma = \frac{1}{\rho} = \frac{ne^2\tau}{m}$	$\mathrm{S\,m^{-1}}$	$[\mathrm{M^{-1}L^{-3}T^3A^2}]$
Electromotive Force (EMF)	ε	$\varepsilon = \frac{dW}{dq} = V_+ + V_-$	V (volt)	$[\mathrm{M^1L^2T^{-3}A^{-1}}]$
Relaxation Time	τ	$\tau = \frac{\lambda_{\text{mfp}}}{v_{\text{th}}}$	s (second)	$[\mathrm{M^0L^0T^1A^0}]$
Temperature Coefficient	α	$\alpha = \frac{R - R_0}{R_0(T - T_0)}$	$\mathrm{K^{-1}}$ or $^\circ\mathrm{C^{-1}}$	$[\mathrm{M^0L^0T^0\Theta^{-1}}]$

BOSONANCE

Final Takeaway for NEET Aspirants

Mastering Current Electricity requires fluid transitions between microscopic formulas (n, e, τ, v_d, μ) and macroscopic circuit laws ($V = IR$, $P = I^2R$, Kirchhoff's rules). Whenever faced with an unfamiliar circuit problem on the examination, check first for bridge symmetries or parallel cell equivalences before setting up multiloop equations. Precision in signs, units, and structural assumptions will ensure a perfect score in this high-scoring unit.